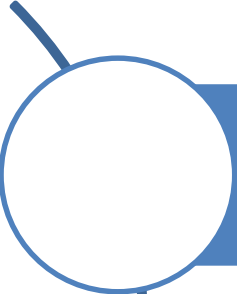



ADVANCED ELECTRICAL CIRCUIT BETI 1333 TRANSFER FUNCTION AND SERIES RESONANCE

Suziana binti Ahmad¹, Halyani binti Mohd Yassim²
1suziana@utem.edu.my, 2halyani@utem.edu.my,

LESSON OUTCOMES

At the end of this chapter, students are able:

-  to describe transfer function and determine characteristics of series resonance
-  to illustrate frequency response of transfer function

SUBTOPICS




Transfer Function




Series Resonance



INTRODUCTION

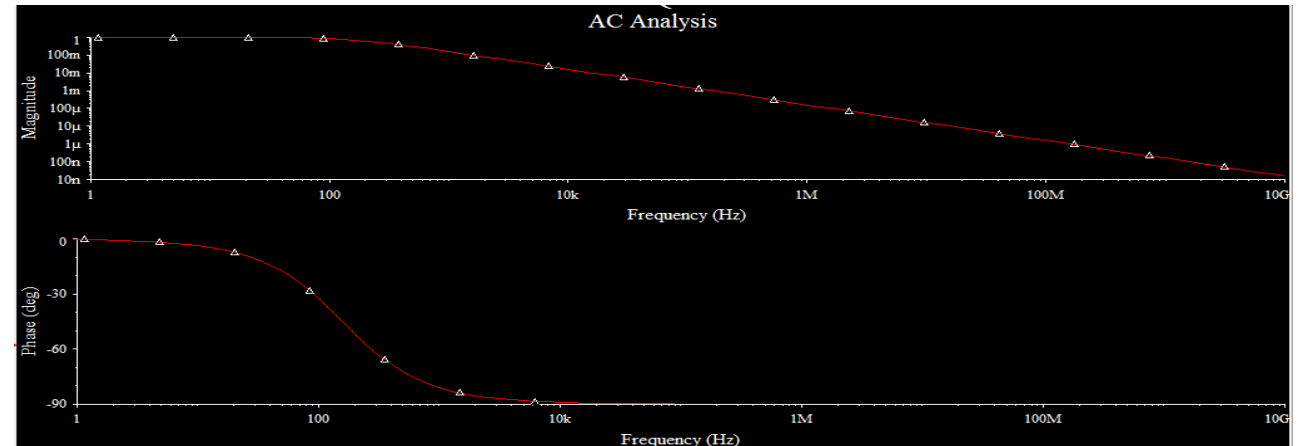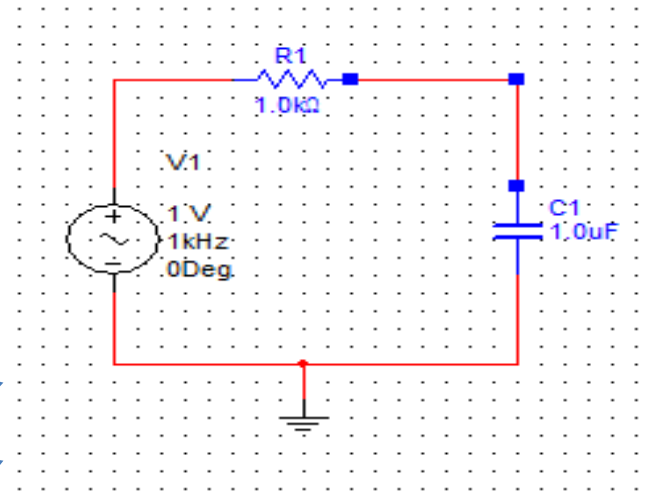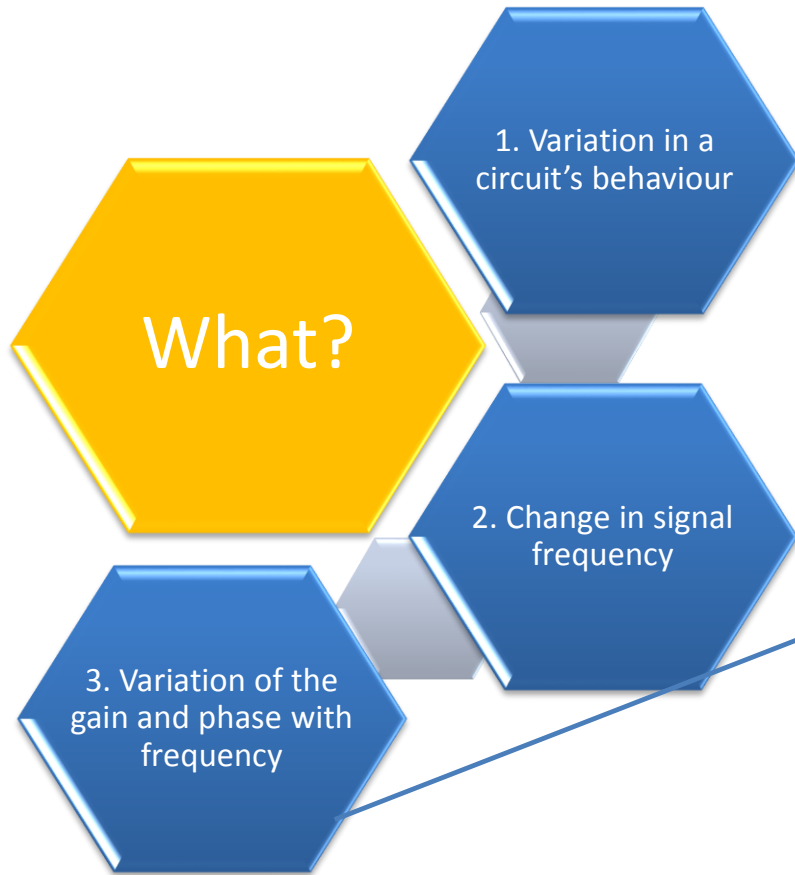

TRANSFER FUNCTION

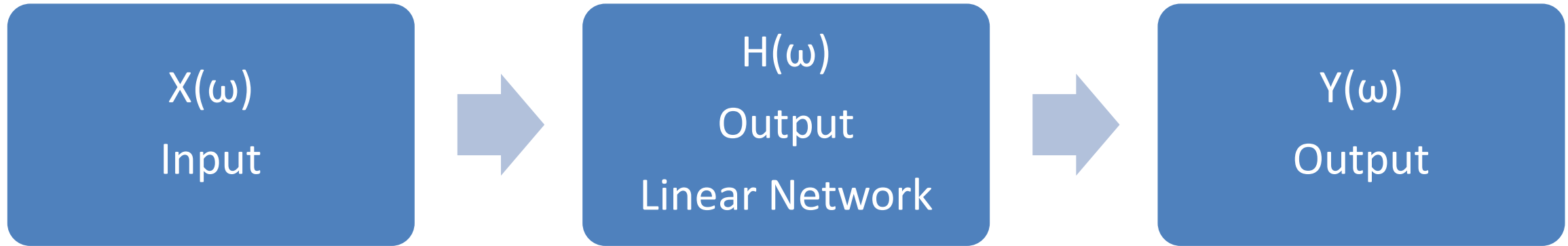

$$\mathbf{H}(\omega) = \frac{\mathbf{Y}(\omega)}{\mathbf{X}(\omega)} = |\mathbf{H}(\omega)| \angle \phi$$

TRANSFER FUNCTION

Voltage gain

$$H(\omega) = \frac{Vo(\omega)}{Vi(\omega)}$$

Current gain

$$H(\omega) = \frac{Io(\omega)}{Ii(\omega)}$$

Transfer impedance


$$H(\omega) = \frac{Vo(\omega)}{Ii(\omega)}$$

Transfer Admittance

$$H(\omega) = \frac{Io(\omega)}{Vi(\omega)}$$

EXAMPLE 1

Find the transfer function V_o/V_i and frequency response of circuit below.

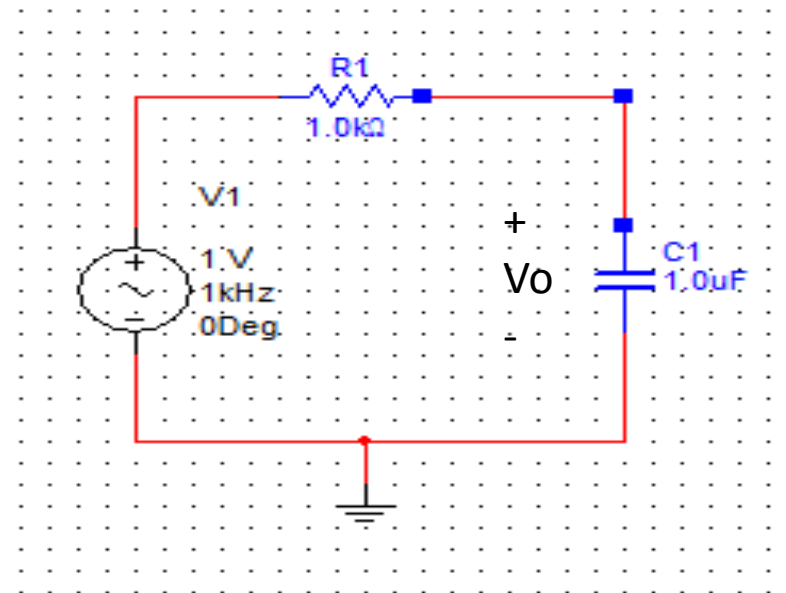

SOLUTION 1

STEP 1 :

The transfer function:

$$H(\omega) = \frac{V_o}{V_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$H(\omega) = \frac{1}{1 + j\omega 0.001}$$

STEP 2 :

The magnitude:

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_o}\right)^2}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{1000}\right)^2}}$$

STEP 3 :

The phase:

$$\phi = -\tan^{-1} \frac{\omega}{\omega_o}$$

$$\phi = -\tan^{-1} \frac{\omega}{1000}$$


$$j\omega RC = j\omega(1\text{k}\Omega)(1\mu\text{F}) = j\omega 0.001$$

Angular frequency:

$$\omega_o = \frac{1}{RC} = \frac{1}{1000\Omega(1\mu\text{F})} = 1000$$


SOLUTION 1

Frequency response for the RC circuit:

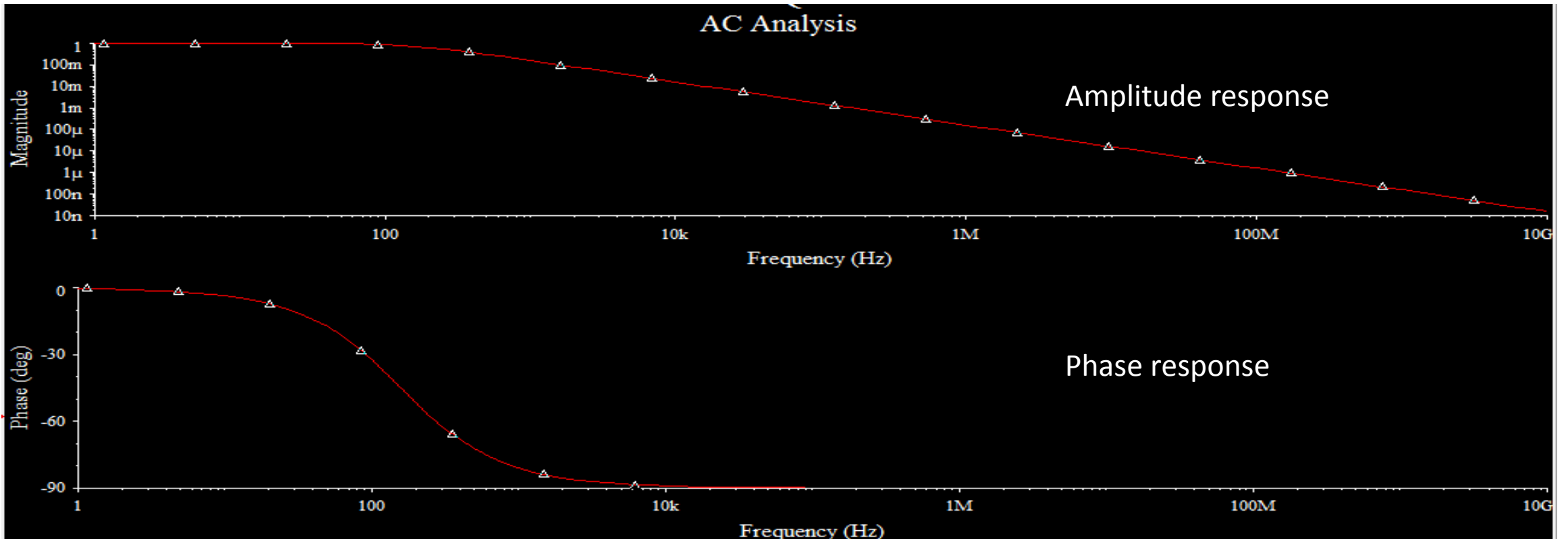

EXAMPLE 2

Find the transfer function V_o/V_i and frequency response of circuit below.

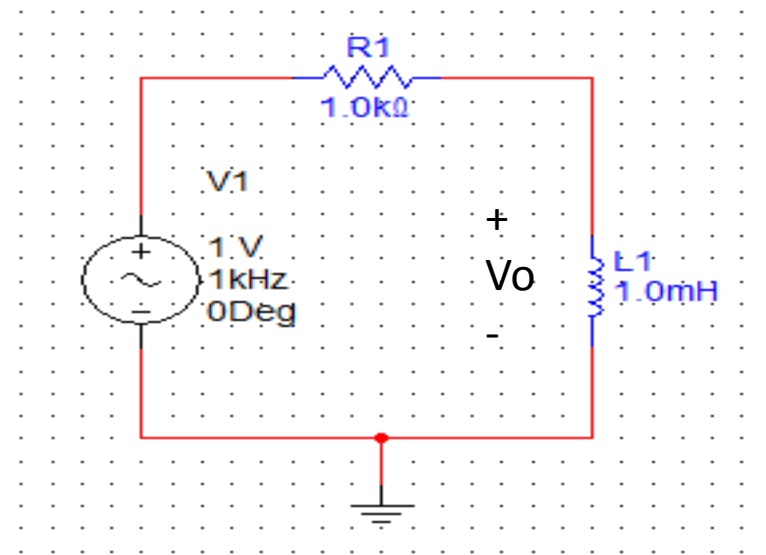

SOLUTION 2

STEP 1 :

The transfer function:

$$H(\omega) = \frac{V_o}{V_i} = \frac{j\omega L}{R+j\omega L} = \frac{1}{1+\frac{R}{j\omega L}}$$

$$H(\omega) = \frac{1}{1+\frac{1000}{j\omega 0.001}}$$

STEP 2 :

The magnitude:

$$|H(\omega)| = \frac{1}{\sqrt{1+(\frac{\omega}{\omega_o})^2}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1+(\frac{\omega}{1000})^2}}$$

STEP 3 :

The phase:

$$\phi = \angle 90^\circ - \tan^{-1} \frac{\omega}{\omega_o}$$


$$\phi = \angle 90^\circ - \tan^{-1} \frac{\omega}{1000000}$$

$$\frac{R}{j\omega L} = \frac{1000}{j\omega 0.001}$$


$$\omega_o = \frac{R}{L} = \frac{1000}{0.001} = 1000000$$

SOLUTION 2


Frequency response for the RL circuit:

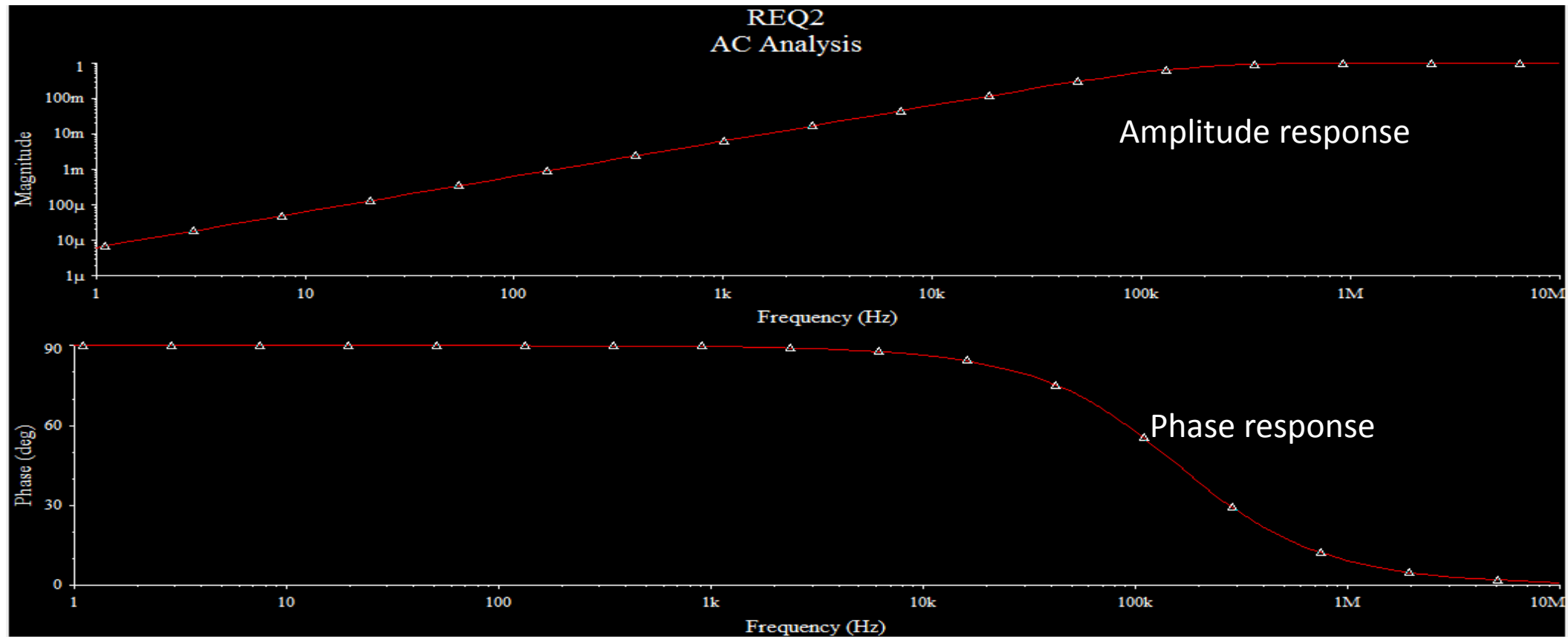

SERIES RESONANCE

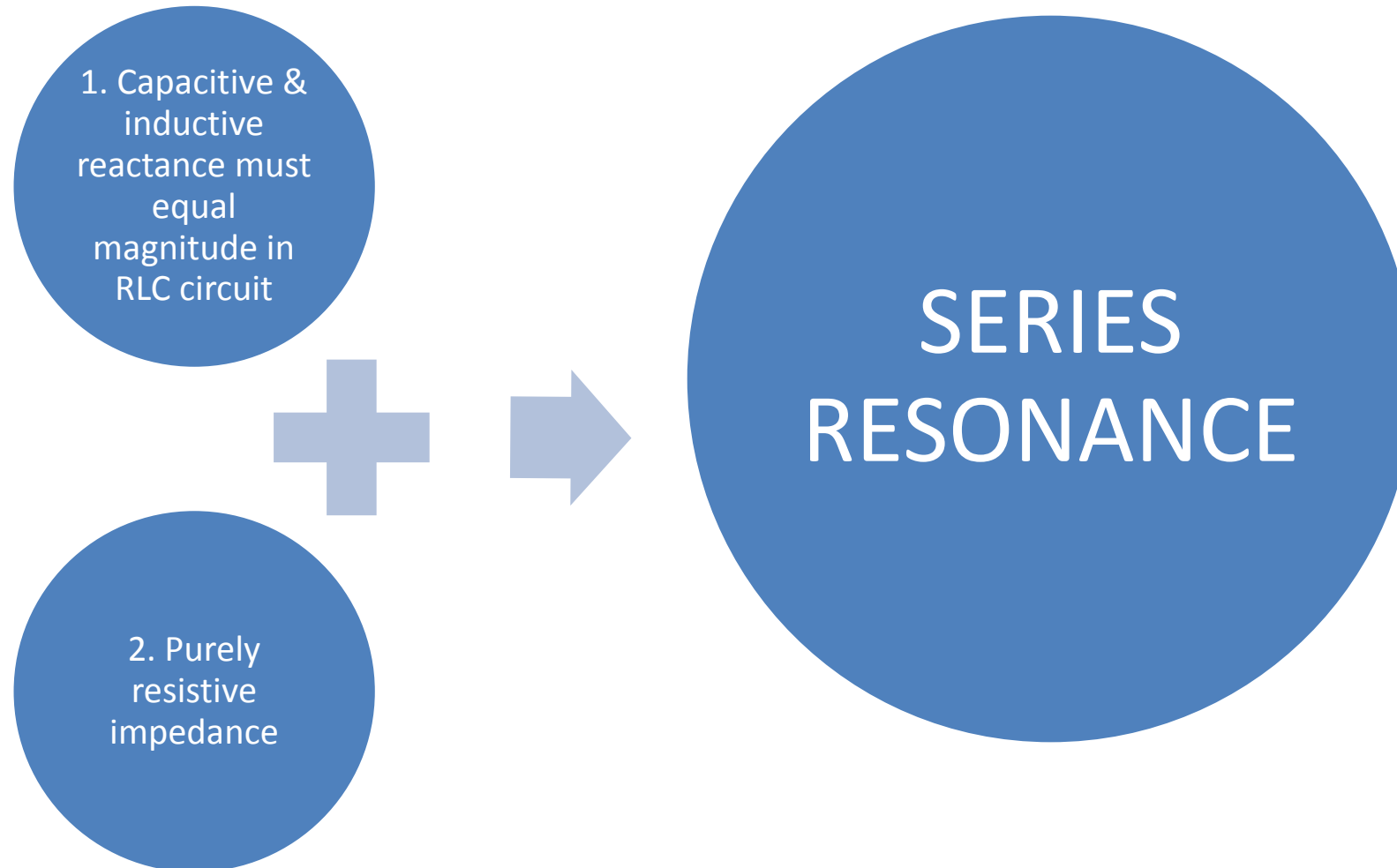

SERIES RESONANCE

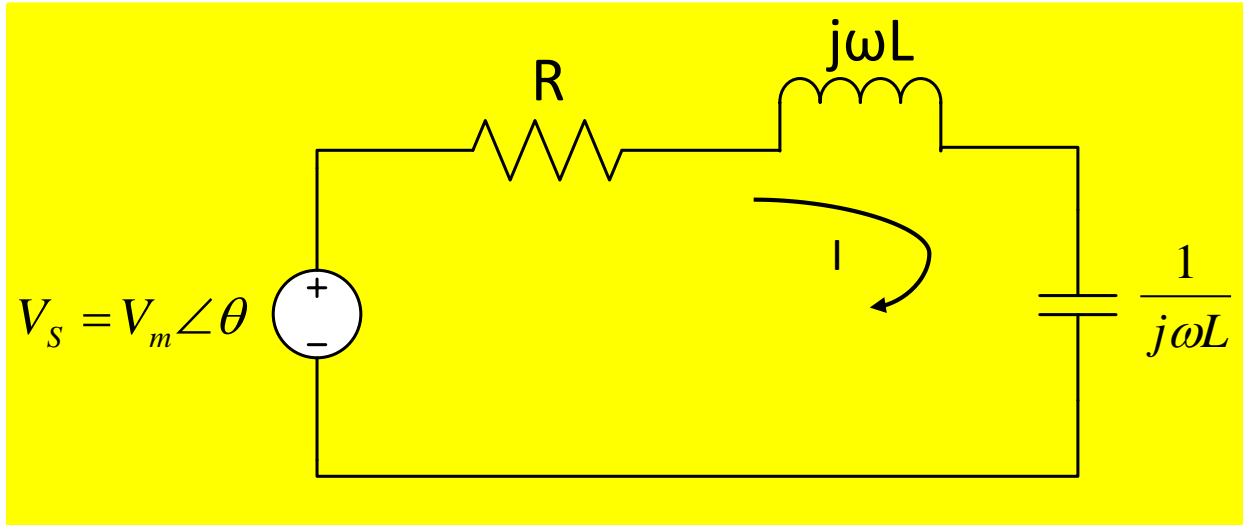


$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

Resonance frequency

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

SERIES RESONANCE

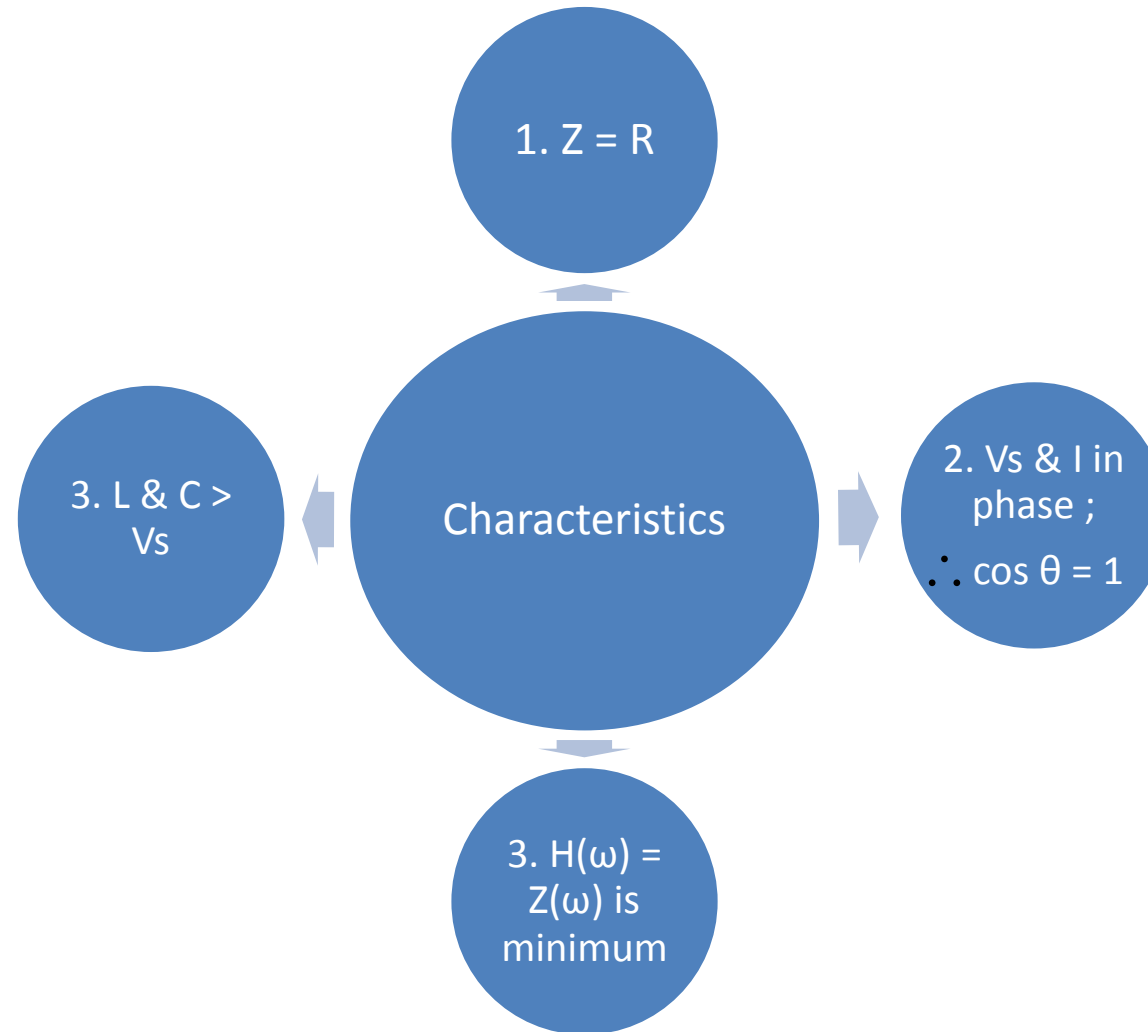

SERIES RESONANCE

Bandwidth (B)

The current's of frequency response is


$$I = |I| = \frac{V_m}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

From RLC circuit, the average power is :

$$P(\omega) = \frac{1}{2} I^2 R$$

So, the highest power dissipated at resonance is :
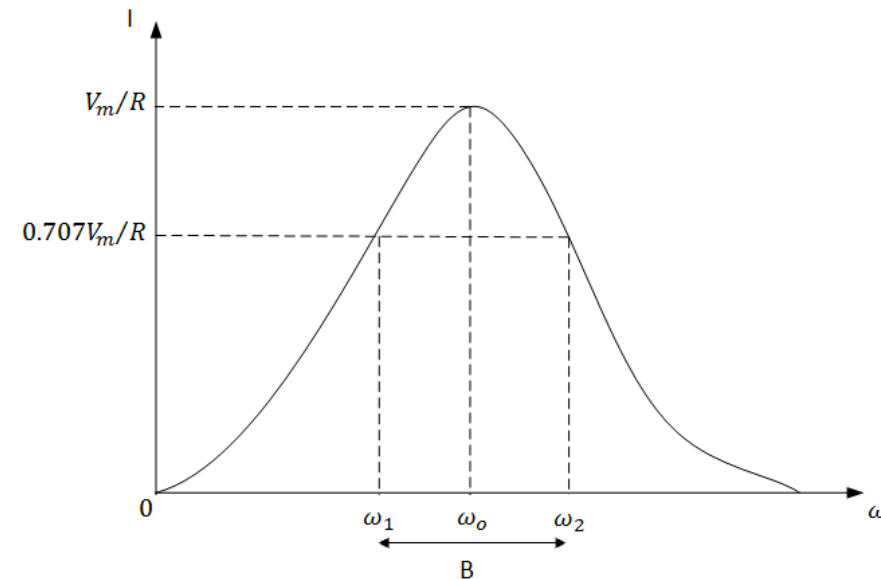
$$P(\omega_o) = \frac{1}{2} \frac{V_m^2}{R}$$



SERIES RESONANCE

→ ω_1 & ω_2 = Half-power frequencies at power dissipated is half the maximum value :

$$P(\omega_1) = P(\omega_2) = \frac{1}{2} \frac{(V_m/\sqrt{2})^2}{R} = \frac{V_m^2}{4R}$$

→ with set up $Z = \sqrt{2}R$, then the half-power frequencies :

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_o = \sqrt{\omega_1 \omega_2}$$

∴ Bandwidth : $B = \omega_2 - \omega_1$

SERIES RESONANCE

Quality factor, Q:

$$Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o CR}$$

Bandwidth, B:

$$B = \frac{R}{L} = \frac{\omega_o}{Q} = \omega_o^2 CR$$

For $Q \geq 10$:

$$\omega_1 = \omega_o - \frac{B}{2}$$

$$\omega_2 = \omega_o + \frac{B}{2}$$

EXAMPLE 3

Given circuit in Figure 1:

- Calculate the resonant frequency
- Find the quality factor and bandwidth
- Determine half power frequencies

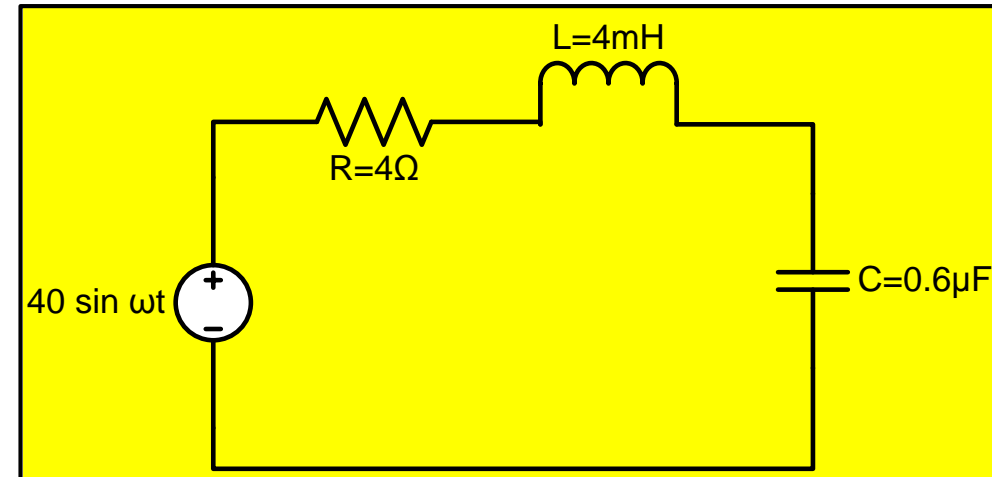


Figure 1

SOLUTION 3

a) Resonant frequency:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\therefore \omega_0 = 20 \text{krad} / \text{s}$$

b) Bandwidth:

$$B = \frac{R}{L}$$

$$\therefore B = 1000 \text{rad} / \text{s}$$

Quality Factor:

$$Q = \frac{\omega_0}{B}$$

$$\therefore Q = 20$$

SOLUTION 3

c) Half-power frequencies:

$$\omega_1 = \omega_0 - \frac{B}{2}$$

$$\therefore \omega_1 = 19.5 \text{krad} / s$$

$$\omega_2 = \omega_0 + \frac{B}{2}$$

$$\therefore \omega_2 = 20.5 \text{krad} / s$$

SELF REVIEW QUESTIONS

1. The transfer function is a ratio of a phasor output to a phasor input.

TRUE

FALSE

2. The impedance for an inductor is _____.

3. Given $R = 5 \Omega$ and $L = 10 \text{ H}$ are arranged in series. What is the angular frequency for this RL circuit?

a) 0.5 s

b) 1 s

c) 2 s

d) 10 s

4. Identify the difference between the half-power frequencies:

a) quality factor

b) resonant frequency

c) bandwidth

d) cutoff frequency

5. Give one (1) of the characteristics in series resonance.

Answer: _____

ANSWERS

1. TRUE
 2. $j\omega L$
 3. a
 4. c
 5. i) $Z = R$
 - ii) V_s & I in phase ; $\cos \theta = 1$
 - iii) $H(\omega) = Z(\omega)$ is minimum
 - iv) inductor (L) & capacitor $C > V_s$
- **choose any of the answer above