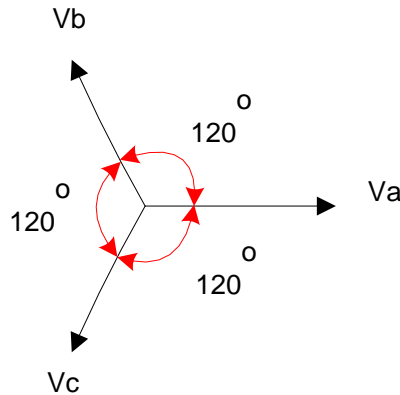


## UNBALANCED THREE-PHASE POWER FLOW

### Definition of balanced system



$$|V_a| = |V_b| = |V_c|$$

If  $|V_a| = |V_b| = |V_c|$  and each other separated by an angle of  $120^\circ$


That is called balanced system. **Otherwise, it is called unbalanced system.**

Balanced system → Single phase load flow

Unbalanced system → Three phase load flow

# Unbalanced three phase power flow based on topology network
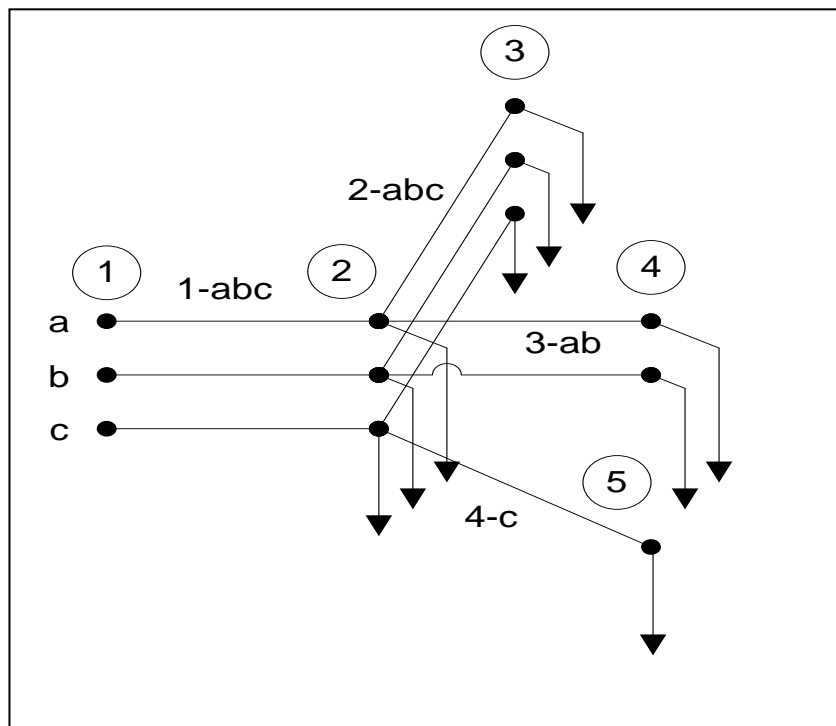
## 1. Building BIBC-Matrix using K-Matrix



Bus \ Branch		Bus ②			Bus ③			Bus ④			Bus ⑤		
		a	b	c	a	b	c	a	b	c	a	b	c
1	a	1	0	0	1	0	0	1	0	0	0	0	0
	b	0	1	0	0	1	0	0	1	0	0	0	0
	c	0	0	1	0	0	1	0	0	0	0	0	1
2	a				1	0	0						
	b				0	1	0						
	c				0	0	1						
3	a							1	0	0			
	b							0	1	0			
	c							0	0	0			
4	a										0	0	0
	b										0	0	0
	c										0	0	1



**K =** [Matrix]



**BIBC Matrix = - [K -Matrix]**

BIBC =

Branch		Bus			
		②	③	④	⑤
		a b c	a b c	a b 0	0 0 c
1	a	$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$	$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$	$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 0 \end{bmatrix}$	$\begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 1 \end{bmatrix}$
	b				
	c				
2	a	$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$	$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$		
	b				
	c				
3	a			$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 0 \end{bmatrix}$	
	b				
	0				
4	0				$\begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 1 \end{bmatrix}$
	0				
	c				
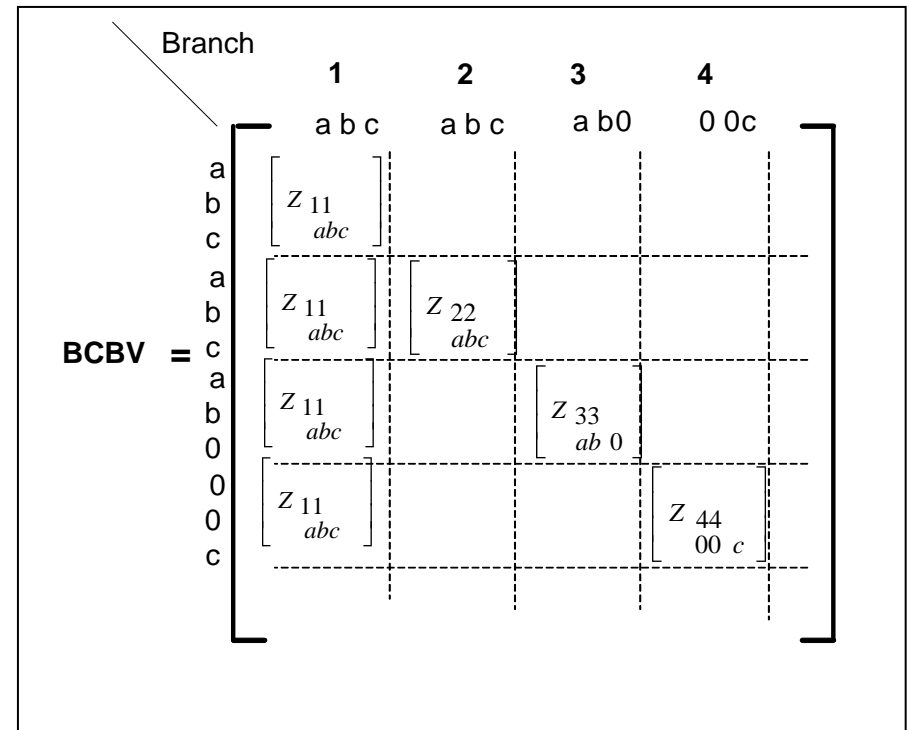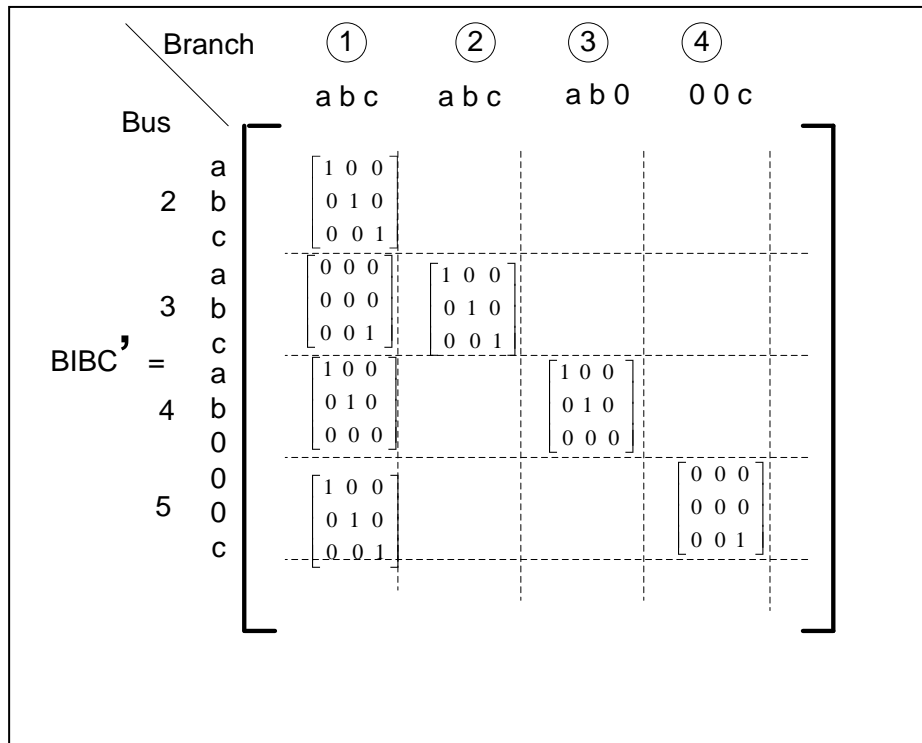
## 2. Building **BCBV** Matrix using transpose of **BIBC** matrix



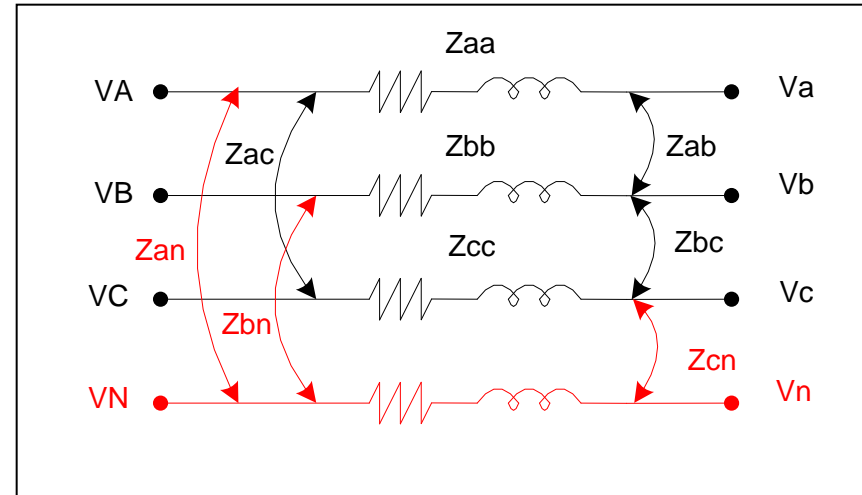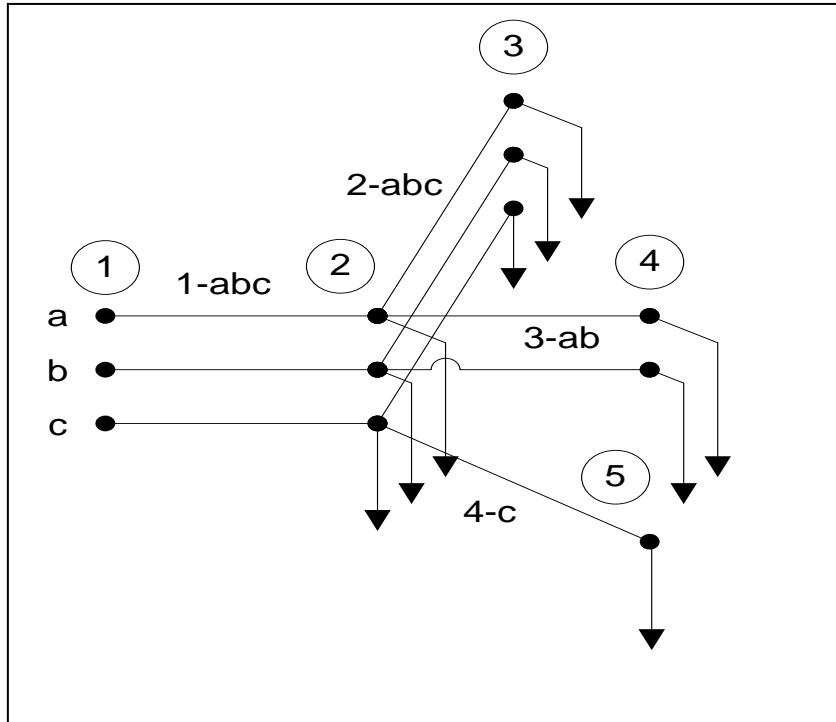


$$[Z_{abc}] = \begin{bmatrix} Z_{aa-n} & Z_{ab-n} & Z_{ac-n} \\ Z_{ba-n} & Z_{bb-n} & Z_{bc-n} \\ Z_{ca-n} & Z_{cb-n} & Z_{cc-n} \end{bmatrix}$$

$$[Z11_{abc}] = \begin{bmatrix} Z_{aa-n} & Z_{ab-n} & Z_{ac-n} \\ Z_{ba-n} & Z_{bb-n} & Z_{bc-n} \\ Z_{ca-n} & Z_{cb-n} & Z_{cc-n} \end{bmatrix}$$

$$[Z22_{abc}] = \begin{bmatrix} Z_{aa-n} & Z_{ab-n} & Z_{ac-n} \\ Z_{ba-n} & Z_{bb-n} & Z_{bc-n} \\ Z_{ca-n} & Z_{cb-n} & Z_{cc-n} \end{bmatrix}$$

$$[Z33_{ab0}] = \begin{bmatrix} Z_{aa-n} & Z_{ab-n} & 0 \\ Z_{ba-n} & Z_{bb-n} & 0 \\ 0 & 0 & 0 \end{bmatrix}$$
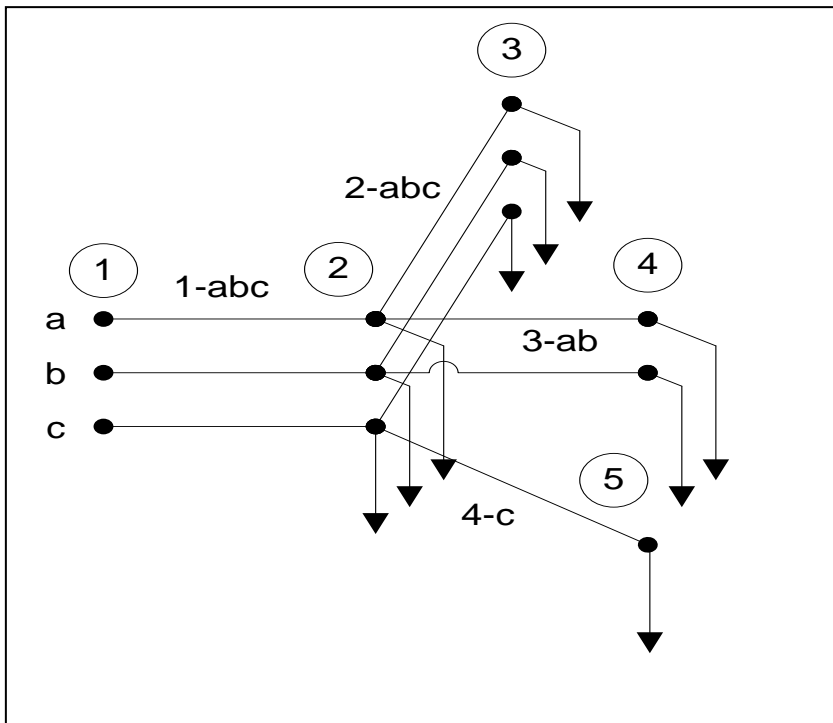
$$[Z44_{00c}] = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & Z_{cc-n} \end{bmatrix}$$



### 3. Follow the algorithm.

1. Input data.
2. Build **BIBC** matrix.
3. Build **BCBV** matrix.
4. Build **DLF** matrix.
5. Iteration  $k=0$ .
6. Iteration  $k=k+1$ .
7. Solve for three-phase power flow by using

$$I_i^k = \left( \frac{P_i + jQ_i}{V_i^k} \right)^*$$

And

$$[\Delta V^k] = [\mathbf{DLF}][I^k]$$

And update voltages.

$$[V^{k+1}] = [V_{bus\_no\ load}] - [\Delta V^k]$$

8. If  $\max_i (|I_i^{k+1}| - |I_i^k|) > tolerance$ , go to (6)
9. Report and end.


EXAMPLE:

Data:

$$Z = \begin{bmatrix} 0.2 + j0.4 & 0 & 0 \\ 0 & 0.2 + j0.4 & 0 \\ 0 & 0 & 0.2 + j0.4 \end{bmatrix} \Omega$$

$$Z1=Z2=Z3=Z$$
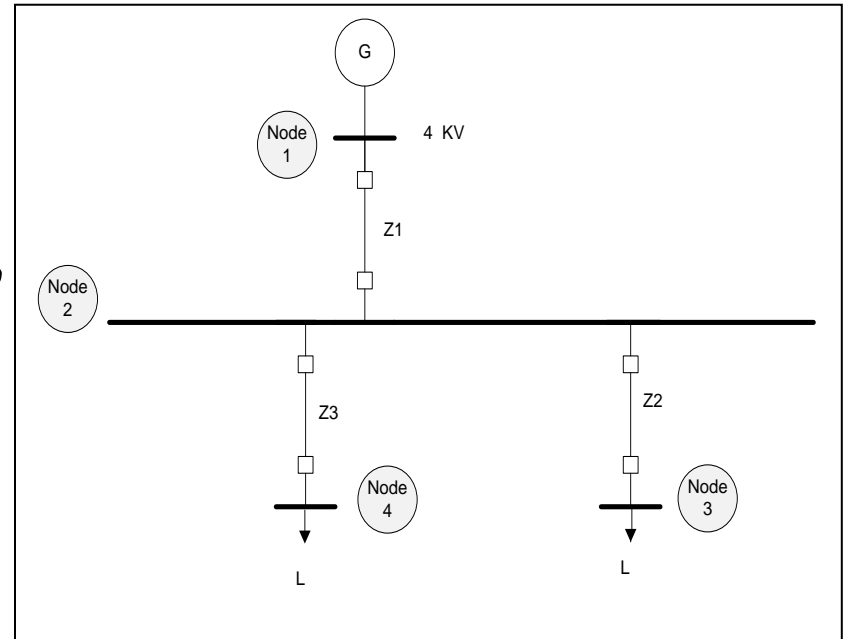
$$L = \begin{bmatrix} 0.2 \text{ MW} + j0.8 \text{ MVar} \\ 0.2 \text{ MW} + j0.8 \text{ MVar} \\ 0.2 \text{ MW} + j0.8 \text{ MVar} \end{bmatrix} \begin{matrix} \textit{phase a} \\ \textit{phase b} \\ \textit{phase c} \end{matrix}$$






Solution:

### 1. Input Data

Define Voltage reference;

$$V_a = 4000 \angle 0^\circ; V_b = 4000 \angle -120^\circ; V_c = 4000 \angle 120^\circ$$
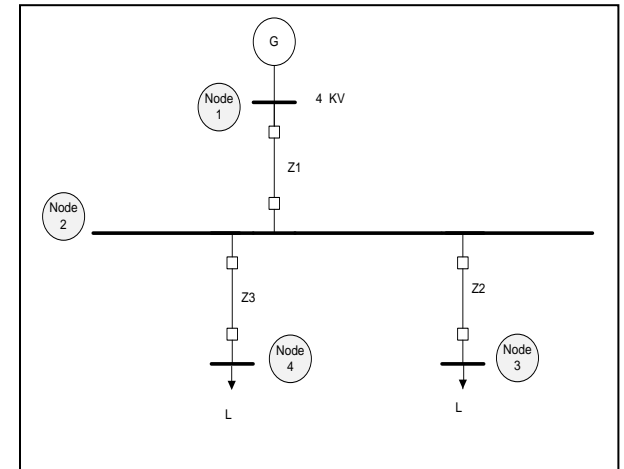
$$V_{bus\_no\ load} = \begin{bmatrix} 4000 \\ -2000 - 3464.1i \\ -2000 + 3464.1i \\ 4000 \\ -2000 - 3464.1i \\ -2000 + 3464.1i \\ 4000 \\ -2000 - 3464.1i \\ -2000 + 3464.1i \end{bmatrix}$$



## 2. Build BIBC

$$K = \begin{bmatrix} -1 & -1 & -1 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \end{bmatrix}$$

$$BIBC = \begin{bmatrix} 1 & 1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

## 3. Build BCBV

$$BCBV = \begin{bmatrix} Z1 & 0 & 0 \\ Z1 & Z2 & 0 \\ Z1 & 0 & Z3 \end{bmatrix}$$

## 4. Build DLF

$$DLF = \begin{bmatrix} Z1 & 0 & 0 \\ Z1 & Z2 & 0 \\ Z1 & 0 & Z3 \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$DLF = \begin{bmatrix} Z1 & Z1 & Z1 \\ Z1 & Z1 + Z2 & Z1 \\ Z1 & Z1 & Z1 + Z3 \end{bmatrix}$$

$$DLF = \begin{bmatrix} Z & Z & Z \\ Z & 2Z & Z \\ Z & Z & 2Z \end{bmatrix}$$

$$DLF = \begin{bmatrix} 0.2 + j0.4 & 0 & 0 & 0.2 + j0.4 & 0 & 0 & 0.2 + j0.4 & 0 & 0 \\ 0 & 0.2 + j0.4 & 0 & Z & 0 & 0.2 + j0.4 & 0 & 0.2 + j0.4 & 0 \\ 0 & 0 & 0.2 + j0.4 & 0 & 0 & 0.2 + j0.4 & 0 & 0 & 0.2 + j0.4 \\ 0.2 + j0.4 & 0 & 0 & 0.4 + j0.8 & 0 & 0 & 0.2 + j0.4 & 0 & 0 \\ 0 & 0.2 + j0.4 & 0 & 0 & 0.4 + j0.8 & 0 & 0 & 0.2 + j0.4 & 0 \\ 0 & 0 & 0.2 + j0.4 & 0 & 0 & 0.4 + j0.8 & 0 & 0 & 0.2 + j0.4 \\ 0.2 + j0.4 & 0 & 0 & 0.2 + j0.4 & 0 & 0 & 0.4 + j0.8 & 0 & 0 \\ 0 & 0.2 + j0.4 & 0 & 0 & 0.2 + j0.4 & 0 & 0 & 0.4 + j0.8 & 0 \\ 0 & 0 & 0.2 + j0.4 & 0 & 0 & 0.2 + j0.4 & 0 & 0 & 0.4 + j0.8 \end{bmatrix}$$

## 5. ITERATION

Calculate I

For the 1<sup>st</sup> iteration V each bus (Vbus) assumed equal to Vref

Iteration, k=1;

$$V_a = 4000 \angle 0^\circ; V_b = 4000 \angle -120^\circ; V_c = 4000 \angle 120^\circ$$

$$I_i^k = \left( \frac{P_i + jQ_i}{V_i^k} \right)^*$$

$$I_{4a}^1 = \left( \frac{(0.2 + j0.8)1e6}{4 * 1e3} \right)^* = \left( \frac{(0.2 - j0.8)1e6}{4 * 1e3 \angle 0^\circ} \right) = 50.00 - 25.00i \text{ A}$$

$$I_{4a}^1 = I_{3a}^1 = 50.00 - 25.00i \text{ A}$$

$$I_{4b}^1 = \left( \frac{(0.2 + j0.8)1e6}{4 * 1e3 \angle -120^\circ} \right)^* = \left( \frac{(0.2 - j0.8)1e6}{4 * 1e3 \angle -120^\circ} \right) = -198.21 + 56.70i \text{ A}$$

$$I_{4b}^1 = I_{3b}^1 = -198.21 + 56.70i \text{ A}$$

$$I_{4c}^1 = \left( \frac{(0.2 + j0.8)1e6}{4 * 1e3 \angle 120^\circ} \right)^* = \left( \frac{(0.2 - j0.1)1e6}{4 * 1e3 \angle 120^\circ} \right) = 148.21 + 143.30i \text{ A}$$

$$I_{4c}^1 = I_{3c}^1 = 148.21 + 143.30i \text{ A}$$

$$I_{2a}^1 = I_{2b}^1 = I_{2c}^1 = 0$$

$$I^1 = \begin{bmatrix} I_{2a}^1 \\ I_{2b}^1 \\ I_{2c}^1 \\ I_{3a}^1 \\ I_{3b}^1 \\ I_{3c}^1 \\ I_{4a}^1 \\ I_{4b}^1 \\ I_{4c}^1 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 50.00 - 25.00i \\ -198.21 + 56.70i \\ 148.21 + 143.30i \\ 50.00 - 25.00i \\ -198.21 + 56.70i \\ 148.21 + 143.30i \end{bmatrix}$$

Calculate  $\Delta V_1$

$$[\Delta V] = [DLF][I]$$

$[\Delta V_1]$	$0.2 + j0.4$	$0$	$0$	$0.2 + j0.4$	$0$	$0$	$0.2 + j0.4$	$0$	$0$	$\begin{bmatrix} 0 \\ 0 \\ 0 \\ 50.00 - 25.00i \\ -198.21 + 56.70i \\ 148.21 + 143.30i \\ 50.00 - 25.00i \\ -198.21 + 56.70i \\ 148.21 + 143.30i \end{bmatrix}$	
	$0$	$0.2 + j0.4$	$0$	$Z$	$0$	$0.2 + j0.4$	$0$	$0$	$0.2 + j0.4$		$0$
	$0$	$0$	$0.2 + j0.4$	$0$	$0$	$0.2 + j0.4$	$0$	$0$	$0.2 + j0.4$		$0$
	$0.2 + j0.4$	$0$	$0$	$0.4 + j0.8$	$0$	$0$	$0.2 + j0.4$	$0$	$0$		$0$
	$0$	$0.2 + j0.4$	$0$	$0$	$0.4 + j0.8$	$0$	$0$	$0.2 + j0.4$	$0$		$0$
	$0$	$0$	$0.2 + j0.4$	$0$	$0$	$0.4 + j0.8$	$0$	$0$	$0.2 + j0.4$		$0$
	$0.2 + j0.4$	$0$	$0$	$0.2 + j0.4$	$0$	$0$	$0.4 + j0.8$	$0$	$0$		$0$
	$0$	$0.2 + j0.4$	$0$	$0$	$0.2 + j0.4$	$0$	$0$	$0.4 + j0.8$	$0$		$0$
	$0$	$0$	$0.2 + j0.4$	$0$	$0$	$0.2 + j0.4$	$0$	$0$	$0.4 + j0.8$		$0$

$\Delta V_1 =$

\* 1.0e+002 \*

- 1.8000 - 0.4000i
- 1.2464 - 1.3588i
- 0.5536 + 1.7588i
- 2.7000 - 0.6000i
- 1.8696 - 2.0383i
- 0.8304 + 2.6383i
- 2.7000 - 0.6000i
- 1.8696 - 2.0383i
- 0.8304 + 2.6383i

Iteration, k=2;

$$V_{i=2:4}^2 = V_{bus\_no\ load} - \Delta V_1$$

$V_{i=2:3}^2$	1.0e+003 *		1.0e+002 *		1.0e+003 *
	4.0000		1.8000 - 0.4000i		3.8200 + 0.0400i
	-2.0000 - 3.4641i		-1.2464 - 1.3588i		-1.8754 - 3.3282i
	-2.0000 + 3.4641i		-0.5536 + 1.7588i		-1.9446 + 3.2882i
	4.0000	-	2.7000 - 0.6000i	=	3.7300 + 0.0600i
	-2.0000 - 3.4641i		-1.8696 - 2.0383i		-1.8130 - 3.2603i
	-2.0000 + 3.4641i		-0.8304 + 2.6383i		-1.9170 + 3.2003i
	4.0000		2.7000 - 0.6000i		3.7300 + 0.0600i
	-2.0000 - 3.4641i		-1.8696 - 2.0383i		-1.8130 - 3.2603i
	-2.0000 + 3.4641i		-0.8304 + 2.6383i		-1.9170 + 3.2003i

$$I_{i=2:4}^2 = \left( \frac{P_{i=2:4} + jQ_{i=2:4}}{V_{i=2:4}^2} \right)^*$$

Using the same way... the results each iterations can be shown in the table:

$I^2$	$I^3$	$I^4$	$I^5$	$I^6$	$I^7$
1.0e+002 *	1.0e+002 *	1.0e+002 *	1.0e+002 *	1.0e+002 *	1.0e+002 *
0	0	0	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0
0.5705 - 2.1356i	0.5737 - 2.1474i	0.5742 - 2.1483i	0.5742 - 2.1483i	0.5742 - 2.1484i	0.5742 - 2.1484i
-2.1348 + 0.5737i	-2.1466 + 0.5769i	-2.1475 + 0.5769i	-2.1476 + 0.5769i	-2.1476 + 0.5769i	-2.1476 + 0.5769i
1.5642 + 1.5619i	1.5729 + 1.5705i	1.5734 + 1.5714i	1.5734 + 1.5714i	1.5734 + 1.5714i	1.5734 + 1.5714i
0.5705 - 2.1356i	0.5737 - 2.1474i	0.5742 - 2.1483i	0.5742 - 2.1483i	0.5742 - 2.1484i	0.5742 - 2.1484i
-2.1348 + 0.5737i	-2.1466 + 0.5769i	-2.1475 + 0.5769i	-2.1476 + 0.5769i	-2.1476 + 0.5769i	-2.1476 + 0.5769i
1.5642 + 1.5619i	1.5729 + 1.5705i	1.5734 + 1.5714i	1.5734 + 1.5714i	1.5734 + 1.5714i	1.5734 + 1.5714i

$V^2$	$V^3$	$V^4$	$V^5$	$V^6$	$V^7$
1.0e+003 *	1.0e+003 *	1.0e+003 *	1.0e+003 *	1.0e+003 *	1.0e+003 *
3.8200 + 0.0400i	3.8063 + 0.0398i	3.8053 + 0.0400i	3.8052 + 0.0400i	3.8052 + 0.0400i	3.8052 + 0.0400i
-1.8754 - 3.3282i	-1.8687 - 3.3163i	-1.8680 - 3.3155i	-1.8679 - 3.3154i	-1.8679 - 3.3154i	-1.8679 - 3.3154i
-1.9446 + 3.2882i	-1.9376 + 3.2765i	-1.9373 + 3.2755i	-1.9372 + 3.2754i	-1.9372 + 3.2754i	-1.9372 + 3.2754i
3.7300 + 0.0600i	3.7095 + 0.0597i	3.7079 + 0.0600i	3.7078 + 0.0600i	3.7077 + 0.0600i	3.7077 + 0.0600i
-1.8130 - 3.2603i	-1.8031 - 3.2424i	-1.8020 - 3.2411i	-1.8019 - 3.2410i	-1.8019 - 3.2410i	-1.8019 - 3.2410i
-1.9170 + 3.2003i	-1.9064 + 3.1827i	-1.9059 + 3.1811i	-1.9058 + 3.1810i	-1.9058 + 3.1810i	-1.9058 + 3.1810i
3.7300 + 0.0600i	3.7095 + 0.0597i	3.7079 + 0.0600i	3.7078 + 0.0600i	3.7077 + 0.0600i	3.7077 + 0.0600i
-1.8130 - 3.2603i	-1.8031 - 3.2424i	-1.8020 - 3.2411i	-1.8019 - 3.2410i	-1.8019 - 3.2410i	-1.8019 - 3.2410i
-1.9170 + 3.2003i	-1.9064 + 3.1827i	-1.9059 + 3.1811i	-1.9058 + 3.1810i	-1.9058 + 3.1810i	-1.9058 + 3.1810i



---

--	--	--	--	--	--